

DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE

Bachelor of Technology (Electronics Engineering) SEMESTER - 2 Winter 2025 (Supply.)

Course :Bachelor of Technology (Electronics Engineering) Branch : Engineering and Technology

Semester : SEMESTER - 2

Subject Code & Name: 24AF1000ES206B - PROGRAMMING FOR PROBLEM SOLVING

Time : 3 Hours]

[Total Marks : 60

Instructions to the Students:

1. Each question carries 12 marks.
2. Question No. 1 will be compulsory and include objective-type questions.
3. Candidates are required to attempt any four questions from Question No. 2 to Question No.6
4. Use of non-programmable scientific calculators is allowed.
5. Assume suitable data wherever necessary and mention it clearly.

Q1. Objective type questions. (Compulsory Question)

12

1. The unit of electrical resistance is:
a) Ohm b) Watt c) Henry d) Farad
2. Which element stores energy in the form of an electric field?
a) Resistor b) Inductor c) Capacitor d) Transformer
3. RMS value of a sinusoidal current is equal to:
a) Peak value b) Peak value / $\sqrt{2}$ c) Average value d) Zero
4. Which machine converts mechanical energy into electrical energy?
a) Motor b) Transformer c) Generator d) Induction motor
5. The working principle of an induction motor is based on:
a) Electromagnetic induction b) Electrostatics
c) Ohm's law d) Coulomb's law
6. CRO is mainly used to measure:
a) Resistance b) Power
c) Frequency and waveform d) Energy
7. Moving coil instruments are:
a) AC instruments b) DC instruments
c) Both AC & DC d) None of these
8. Digital Storage Oscilloscope is mainly used to:
a) Measure DC voltage only b) Display waveform and frequency
c) Measure current only d) Measure resistance
9. The total resistance of three resistors 2 Ω , 3 Ω , and 6 Ω connected in series is:
a) 11 Ω b) 1 Ω c) 6 Ω d) 3 Ω
10. Kirchhoff's Current Law (KCL) is based on:
a) Conservation of energy b) Conservation of charge
c) Ohm's law d) Lenz's law
11. Power factor in a purely resistive AC circuit is:
a) 0 b) 0.5 c) 1 d) -1

12. A Series DC motor is suitable for:
a) Constant speed applications b) High starting torque applications
c) Precision speed control d) Low power applications

Q2. Solve the following.

- A) Explain the Kirchhoff Current Law with a suitable example. 6
B) Derive an expression for the average and the RMS value in an AC circuit. 6

Q3. Solve the following.

- A) Distinguished between Motors and Generators with examples. 6
B) Derive the EMF equation for a transformer with a neatly labelled diagram. 6

Q4. Solve Any Two of the following.

- A) Explain the principle operation of a PN Junction Diode with a suitable diagram. 6
B) Explain the working of a full-wave bridge rectifier with waveforms. 6
C) Explain the functional block diagram of a DC power supply. 6

Q5. Solve Any Two of the following.

- A) Derive the relation between current gains in Common Base (α) and Common Emitter (β) configurations. 6
B) Explain the input and output characteristics of a BJT in the Common Emitter (CE) configuration. 6
C) Enlist Different Transistor Biasing Techniques, and explain the Fixed Biased Technique in detail. 6

Q6. Solve Any Two of the following.

- A) Explain the block Diagram of a function Generator. 6
B) Describe the working principle of the Moving Coil instruments with a suitable diagram. 6
C) Explain the operation of a Digital Storage Oscilloscope with suitable Diagram. 6

*** End ***