

Q.4	Solve Any Two of the following.		12
A)	Compare Characteristics of TTL, CMOS, ECL, RTL, I2L and DCTL logic families.	(3)	6
B)	Define and explain: i) Fan in and Fan out ii) Noise immunity iii) Propagation Delay	(1,2)	6
C)	Explain in brief the operation of CMOS NAND Gate with schematic diagram.	(3)	6
Q. 5	Solve Any Two of the following.		12
A)	Implement given Boolean functions using PLA, PAL and PROM F1 (A,B,C)= $\sum m(0, 2,6,7)$ F2(A,B,C)= $\sum m(1, 3,4,5,7)$	(4)	6
B)	Write VHDL code for Mux 4:1 using dataflow and behavioural architecture style.	(4)	6
C)	Classify memories RAM and ROM.	(3)	6
	*** End ***		

The grid and the borders of the table will be hidden before final printing.