

Course: B. Tech.      Branch: Electronics and Communication Engineering /  
 Electronics and Telecommunication Engineering      Semester: IV  
 Subject Code & Name: Network Theory (BTETC401)


Max Marks: 60      Date: 16-01-24      Duration: 3 Hr.

**Instructions to the Students:**


1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in ( ) in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

|                                             |            |           |
|---------------------------------------------|------------|-----------|
|                                             | (Level/CO) | Marks     |
| <b>Q. 1 Solve Any Two of the following.</b> |            | <b>12</b> |

- |                                                                                                                                 |            |          |
|---------------------------------------------------------------------------------------------------------------------------------|------------|----------|
| A) State Superposition theorem and find the current passing through the 3 Ω resistor in the circuit using superposition theorem | <b>CO1</b> | <b>6</b> |
|---------------------------------------------------------------------------------------------------------------------------------|------------|----------|

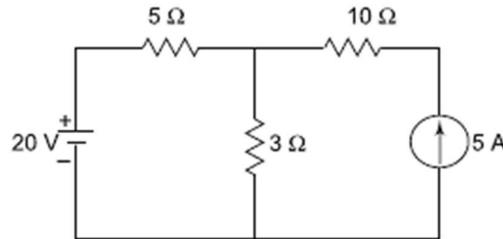

- |                                                                                                    |            |          |
|----------------------------------------------------------------------------------------------------|------------|----------|
| B) Replace the given network shown in Fig by a single current source in parallel with a resistance | <b>CO1</b> | <b>6</b> |
|----------------------------------------------------------------------------------------------------|------------|----------|

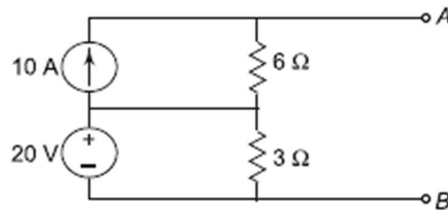


- |                                                                                                                                         |            |          |
|-----------------------------------------------------------------------------------------------------------------------------------------|------------|----------|
| C) Define the terms: TREE AND CO-TREE, Obtain the incidence matrix A from the following reduced incidence matrix A1 and draw its graph. | <b>CO1</b> | <b>6</b> |
|-----------------------------------------------------------------------------------------------------------------------------------------|------------|----------|


$$[A_1] = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & 0 & 0 & -1 & 1 \end{bmatrix}$$

|                                            |           |
|--------------------------------------------|-----------|
| <b>Q.2 Solve Any Two of the following.</b> | <b>12</b> |
|--------------------------------------------|-----------|

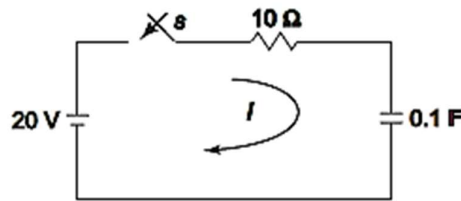- A) A series RC circuit consists of resistor of  $10\ \Omega$  and capacitor of  $0.1\text{ F}$  as shown in Fig. A constant voltage of  $20\text{ V}$  is applied to the circuit at  $t = 0$ . Obtain the current equation. Determine the voltages across the resistor and the capacitor. CO1, CO3 6




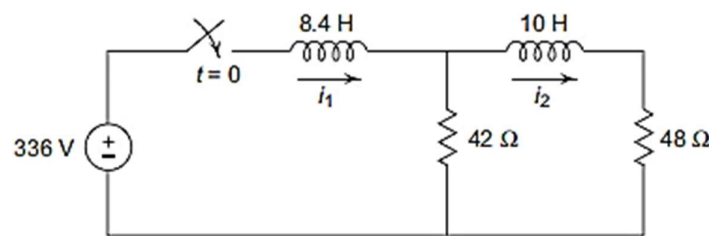- B) Derive an expression for Dc response of an R-L circuit CO1, CO3 6
- C) Obtain the expression for  $i_1$  and  $i_2$  in the circuit shown in Fig. when dc voltage source is applied suddenly. Assume that the initial energy stored in the circuit is zero. CO1, CO3 6




**Q.3 Solve Any Two of the following.** 12

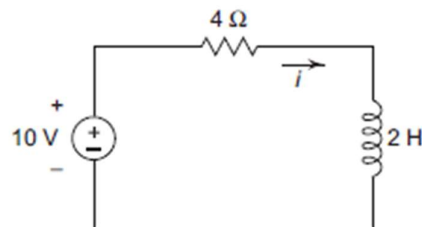- A) Write Laplace transform of some standard Network Functions. CO1, CO3 6
- B) Explain Circuit elements in the s-domain CO1, CO3 6
- C) Determine the current  $i$  for  $t \geq 0$  if initial current  $i(0) = 1$  for the circuit shown in Fig. CO1 6



**Q.4 Solve Any Two of the following.** 12

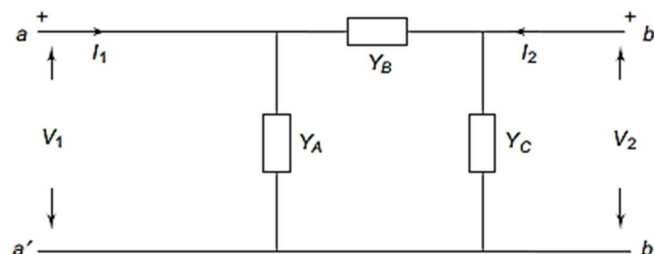- A) Find the Y parameters for the network shown in Fig. CO1, CO4 6




- B)** In the two-port network, compute h-parameters from the following data: **CO1, CO4** **6**
- (a) With the output port short-circuited:  $V_1 = 25 \text{ V}$ ,  $I_1 = 1 \text{ A}$ ,  $I_2 = 2 \text{ A}$
- (b) With the input port open-circuited:  $V_1 = 10 \text{ V}$ ,  $V_2 = 50 \text{ V}$ ,  $I_2 = 2 \text{ A}$
- C)** Derive Z-parameter in terms of Y-parameter, h-parameter and ABCD parameter **CO1, CO4** **6**

**Q. 5 Solve Any Two of the following.** **12**

- A)** Find the two Cauer realisations of driving point function given by **CO1, CO3** **6**

$$Z(S) = \frac{10S^4 + 12S^2 + 1}{2S^3 + 2S}$$

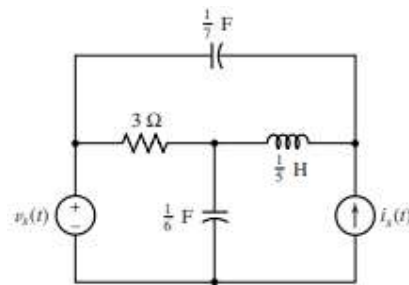- B)** Obtain the normal-form equations for the circuit of Fig., a four-node circuit containing two capacitors, one inductor, and two independent sources. **CO1, CO3** **6**



- C)** Explain about classification of filters. Draw the characteristics of Low-pass filters. **CO1, CO3** **6**

**\*\*\* End \*\*\***