


Instructions to the Students:

1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly in the answer sheet.

(Level/CO) Marks


Q. 1 Solve any two of the followings.

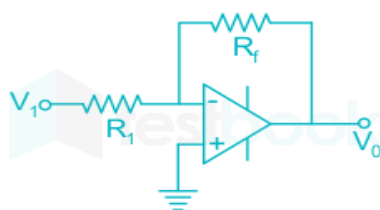- A) Explain the block diagram of op-amp? **Level 1** **6**
- B) Define: i) CMRR ii) Gain iii) Slew rate **Level 1** **6**
- C) If $V_{in}=2V$, $R_1= 200K\Omega$ and $R_f=500K\Omega$, find the output voltage of an Op-Amp. **Level 2** **6**



Q.2 Solve any two of the followings.

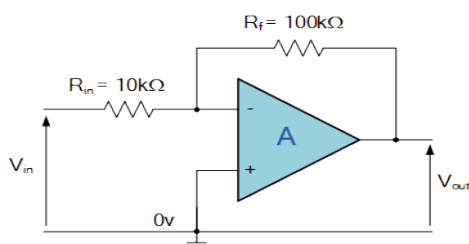- A) Find the closed loop gain of the following inverting amplifier circuit. **Level 3** **6**



- B) Discuss the application of an Op-Amp as a differentiator? **Level 2** **6**
- C) Explain Clippers and Clampers using Op-Amp. **Level 1** **6**

Q. 3 Solve any two of the followings.

- A) With suitable diagrams, explain a summing amplifier using Op-amp. **Level 1** **6**

- | | | |
|---|----------------|----------|
| B) Explain the concept of a non-inverting amplifier and virtual ground in Op-Amp. | Level 1 | 6 |
| C) Design a circuit using Op-amp that provides a gain of 5.5. Assume $R_i = 10k\Omega$, what value would you choose for R_f ? | Level 2 | 6 |

Q.4 Solve any two of the followings.

- | | | |
|---|----------------|----------|
| A) $R = 10\ k$, $v_1 = 2.011V$, and $v_2 = 2.017V$. If R_G is adjusted to $500\ \Omega$, determine: (a) The voltage gain, (b) The output voltage v_o . | Level 1 | 6 |
| B) Define active filter and discuss its classification? | Level 1 | 6 |
| C) Explain the construction and working of a relaxation oscillator. | Level 1 | 6 |

Q. 5 Solve any two of the followings.

- | | | |
|---|----------------|----------|
| A) Compare RC oscillators with LC oscillators. | Level 1 | 6 |
| B) Explain the working of Hartley oscillator with neat diagram. | Level 2 | 6 |
| C) Explain the concept of a weighted resistor. List its advantages, disadvantages. | Level 1 | 6 |

***** End *****